

Digital Design Group Project EENG 28010

Sequential Logic: Latch vs Flip-flop


Dr. Faezeh Arab Hassani
Department of Electrical and Electronic Engineering



Outline

- ❑ Combinational versus Sequential Logic
- ❑ D-Latch vs D-Flip-flop
- ❑ Inferring Combinational or Sequential Logic

Combinational versus Sequential Logic

 

- At any point in time, the output is related to the current input signals
- Output is not only a function of the current input data, but also of previous values
- Includes a combinational logic portion and a module that holds the state
- No intentional connection between the state outputs and inputs
- Example circuits are registers, counters, oscillators, and memory

Outline

- ❑ Combinational versus Sequential Logic
- ❑ D-Latch vs D-Flip-flop
- ❑ Inferring Combinational or Sequential Logic


Value Holders in VHDL vs Hardware

- | | |
|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <ul style="list-style-type: none"> ❑ Value holders in VHDL: <ul style="list-style-type: none"> – Signal – Variable – Constant ❑ Inferring Combinational Logic <ul style="list-style-type: none"> – Value is always written before being read – Assigned in every branch of a conditional structure (case, if-then-else) ❑ Inferring Sequential Logic <ul style="list-style-type: none"> – Read before written – Not assigned in each branch – Control condition <ul style="list-style-type: none"> • Under the control of a level-sensitive condition • Under the control of an edge-sensitive condition | <ul style="list-style-type: none"> ❑ Value holders in hardware: <ul style="list-style-type: none"> – Combinational Gates – Flip-flop – Latch |
|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|

} Sequential
gates
(memory)

D-Latch vs D-Flip-flop

 - A latch is a level-sensitive device, whereas a flip-flop is an edge-triggered device.



- Disadvantages of using latches:


- Timing problems
- Most of the time they are inferred unintentionally
- It's possible for a latch-based circuit to simulate correctly, but not work in real hardware, because the timing delays on the real hardware don't match those predicted in synthesis

Outline

- ❑ Combinational versus Sequential Logic
- ❑ D-Latch vs D-Flip-flop
- ❑ **Inferring Combinational or Sequential Logic**

Inferring Combinational Logic – Eg:

 
```
SIGNAL a, b, c, d: BIT;  
---  
PROCESS(a, b, c)  
  VARIABLE x: BIT;  
BEGIN  
  x := a AND b;  
  d <= x OR c;  
END PROCESS;
```



- ❑ VHDL semantics require that x retains its value over the entire simulation run
- ❑ However x is assigned before reading and used immediately
- ❑ Not necessary to store the value of x in a memory element
- ❑ d is always assigned and never read; memory not needed

Ambiguous Statements
 
```
SIGNAL a, b, c, d: BIT;
---
PROCESS(a, b, c)
  VARIABLE x: BIT;
BEGIN
  d <= x OR c;
  x := a AND b;
END PROCESS;
```



- ☐ VHDL semantics require that x retains its value over the entire simulation run
- ☐ X is read before assigned
- ☐ Hence x has to hold its value during repeated executions of process
- ☐ Infers memory
- ☐ However not clear how to build a latch/flip-flop since x is not assigned under control of any condition
- ☐ Will result in error or warning
- ☐ Simulation results may differ between pre- and post-synthesis

Inferring a Latch

```
ENTITY what IS
PORT (clk, d: IN std_logic;
      q: out std_logic);
END what;

ARCHITECTURE behav OF what IS
BEGIN
  PROCESS(clk, d)
  BEGIN
    IF clk = '1' THEN
      q <= d;
    END IF;
  END PROCESS;
END behav;
```

- ❑ VHDL semantics require that q retains its value over the entire simulation run
- ❑ Not assigned in each branch
- ❑ Latch inferred as assignment is under the control of a level-sensitive condition

Do not use latches!


Mistakenly Inferring Latches with CASE

- ❑ Not assigning all conditional expressions in a CASE structure can lead to latches being inferred (similar to IF situation)

```
library IEEE;
use IEEE.std_logic_1164.all;

ENTITY mux3_seq is
  PORT(a : IN std_logic;
        b : IN std_logic;
        c : IN std_logic;
        sel : IN std_logic_vector(1 DOWNTO 0);
        y : OUT std_logic);
END mux3_seq;
```
 
```
ARCHITECTURE behavior OF mux3_seq IS
  BEGIN
    comb : PROCESS(a,b,c,sel)
    BEGIN
      CASE sel IS
        WHEN "00" => y <= a;
        WHEN "01" => y <= b;
        WHEN "10" => y <= c;
        WHEN OTHERS => --empty
      END CASE;
    END PROCESS comb;
  END behavior;
```




Avoiding Unwanted Latches

- Assigning values of “don’t care” (‘-’) in these cases can avoid unwanted latch inference

```
library IEEE;
use IEEE.std_logic_1164.all;

ENTITY mux3 is
  PORT(a : IN std_logic;
        b : IN std_logic;
        c : IN std_logic;
        sel : IN std_logic_vector(1 DOWNTO 0);
        y : OUT std_logic);
END mux3;

 ARCHITECTURE behavior OF mux3 IS
  BEGIN
    comb : PROCESS(a,b,c,sel)
    BEGIN
      CASE sel IS
        WHEN "00" => y <= a;
        WHEN "01" => y <= b;
        WHEN "10" => y <= c;
        WHEN OTHERS => y <= '-';
      END CASE;
    END PROCESS comb;
  END behavior;
```



Edge Sensitive D Flip-Flop

- ❑ Assignment on rising or falling edge of control signal (Clock)
 - **rising_edge()** and **falling_edge()** functions can be used to specify clock edge
- ❑ Memory inferred because “d” is not assigned for all cases


```

library IEEE;
use IEEE.std_logic_1164.all;

ENTITY d_ff IS
  PORT(d      : IN  std_logic;
        clk    : IN  std_logic;
        q      : OUT std_logic;
        qn     : OUT std_logic);
END d_ff;

ARCHITECTURE behavior OF d_ff IS
  BEGIN
    seq : PROCESS(clk)
      BEGIN
        IF(rising_edge(clk)) THEN
          q <= d;
        END IF;
      END PROCESS seq;
    qn <= not q;
  END behavior;

```

 

Edge Sensitive D Flip-Flop with Synchronous Reset


- ❑ Synchronous reset, so only clk in sensitivity list
- ❑ Memory inferred because “d” is not assigned for all cases

```

library IEEE;
use IEEE.std_logic_1164.all;

ENTITY d_ff IS
    PORT(d : IN std_logic;
         clk : IN std_logic;
         q : OUT std_logic);
END d_ff;

 ARCHITECTURE behav OF FlipFlop IS
BEGIN
    PROCESS(clk)
    BEGIN
        IF clk'event AND clk = '1' THEN
            IF reset = '0' THEN
                q <= '0';
            ELSE
                q <= d;
            END IF;
        END IF;
    END PROCESS;
END behav;
  
```



Edge Sensitive D Flip-Flop with Asynchronous Reset

- ❑ The only signals in the process sensitivity list other than CLOCK should be asynchronous signals
- ❑ Memory inferred because “d” is not assigned for all cases


```

library IEEE;
use IEEE.std_logic_1164.all;

ENTITY d_ff IS
    PORT(d : IN std_logic;
         clk : IN std_logic;
         q : OUT std_logic);
END d_ff;

ARCHITECTURE behav OF FlipFlop IS
BEGIN
    PROCESS(clk, reset)
    BEGIN
        IF reset = '0' THEN
            q <= '0';
        ELSIF clk'event AND clk = '1' THEN
            q <= d;
        END IF;
    END PROCESS;
END behav;

```

 

Latches by stealth: How not to write VHDL

```
.....  
CASE curentState IS  
.....  
WHEN updateState =>  
    tx_reg <= rx;  
    WHEN inputReady =>  
        -- tx_reg is not assigned in any other branch  
        -- instead, its read here  
        if (tx_reg = "11111111")  
            -- do something  
        .....
```

- ☐ Assume that tx_reg should only be updated in state updateState, and the value needs to be read in other states
- ☐ Not assigned in every branch, level-sensitive control condition
- ☐ Results in latches

Let's assume that for this design to work, the value of tx_reg should only be updated in state updateState, and the value needs to be read in other states, i.e. memory is needed. Written in this form, a latch is implied, as the assignment is under the control of a level-sensitive condition, and it is not assigned in every branch. A latch being implied is bad enough, but this is implication by stealth, it does not follow a latch template. This code is unlikely to work even in simulation. It is guaranteed not to work when synthesised.

Avoiding Latches by Stealth

```
regSync : PROCESS (clk)
BEGIN
  IF clk'EVENT AND clk='1' THEN
    IF reset='1' THEN
      tx_reg <= X"FF"; -- assign a HEX value to std_logic_vector
    ELSIF currentState = updateState THEN
      tx_reg <= rx;
    END IF;
  END IF;
END PROCESS; -- regSync
```

- ❑ Separate Process for the memory element
- ❑ Everything that happens inside the process body is predicated upon a clock edge (including the synchronous reset; could also be asynchronous reset)

Avoiding Latches

- ❑ Where do these evil latches come from?
 - You directly instantiated them or inferred them in your code on purpose
 - Valid technique for meeting timing requirements in aggressive designs (eg: borrowing time from the next cycle)
 - DO NOT PRACTICE IN THIS UNIT!
 - You inferred them in your code by accident
 - In processes modelling combinational logic, all the signals on RHS of assignment must appear in sensitivity list.
 - In processes modelling combinational logic, you have incompletely specified if-else or case statements, or read before assigning.
 - In processes modeling sequential logic, you have more than a single clock and asynchronous control in the sensitivity list.